



Technion – Israel Institute of Technology

Electrical Engineering Department – VLSI Lab

# Fast Asynchronous Shift Register for Bit-Serial Communication

Rostislav (Reuven) Dobkin  
Dr. Ran Ginosar, Dr. Avinoam Kolodny

ASYNC06




# Presentation Outline

- On-Chip Communication Challenges
- Fast Asynchronous Serial Communication
  - Transmitter
  - Channel
  - Receiver
- High Data Rate Asynchronous Shift Register
- Performance
- Conclusions



# A Future SoC + NoC Structure

 




# On-Chip Communication Challenges

- Low Power
- High Throughput (bit-per-second)
- Low-Latency Synchronization
- Total Low Latency (fly time from source to sink)
- Low Area (routability)
- High Reliability




# Parallel NoC Links and SoC Buses

 


- Constructed of multiple wires and repeaters
- Incur high leakage power (line drivers and repeaters)
- Often have low utilization (leakage again)
- Occupy large chip area (routing difficulty)
- Incur cross-coupling (delay matching & skew problems)
- Present a significant capacitive load



# Bit-Serial Interconnect

 

 - Fewer lines, fewer line drivers and fewer repeaters



- Reduced leakage power
- Reduced chip area
- Better routability
- Reduced coupling

**BUT**


- Should work N times faster!

$$F_{\text{SER}} = N \times F_{\text{PAR}}$$


 
# Fast Serial Interconnect


- Synchronous Approach:
  - Source-synchronous, with Clock Data Recovery (CDR)
  - Problem: CDR power and area



- Asynchronous Approach:
  - Normal methods are too slow
  - *We consider a faster one*



# Serial Link – Top Structure

 


- Transition signaling instead of sampling: two-phase NRZ Level Encoded Dual Rail (LEDR) asynchronous protocol
- Acknowledge per word instead of per bit
- Wave-pipelining over channel
- Differential encoding
- Low-latency synchronizers




 
# Encoding – Two Phase NRZ LEDR

- Two Phase Non-Return-to-Zero Level Encoded Dual Rail
  - “delta” encoding (one transition per bit)






# Seeking Highest Speed


- No “spacers” (NRZ)
- One transition per bit
- Fast signaling
  - Targeted Speed: One gate delay between bits
    - For 65nm technology this results in 67 Gbps

One Gate Delay  
=  
FO4 INV Delay

 



# Transmitter – Top Architecture

 

- Main Functions:


- Synchronizer (Standard, LDL)
- Dual-Rail Two-Phase Encoder (AFSM)
- Serializer (A Novel Solution)
- Differential Encoder (Differential Driver)

**Fast Serial  
Operation**

**Slow Parallel  
Operation**




# Serializer – Fast SR Approach

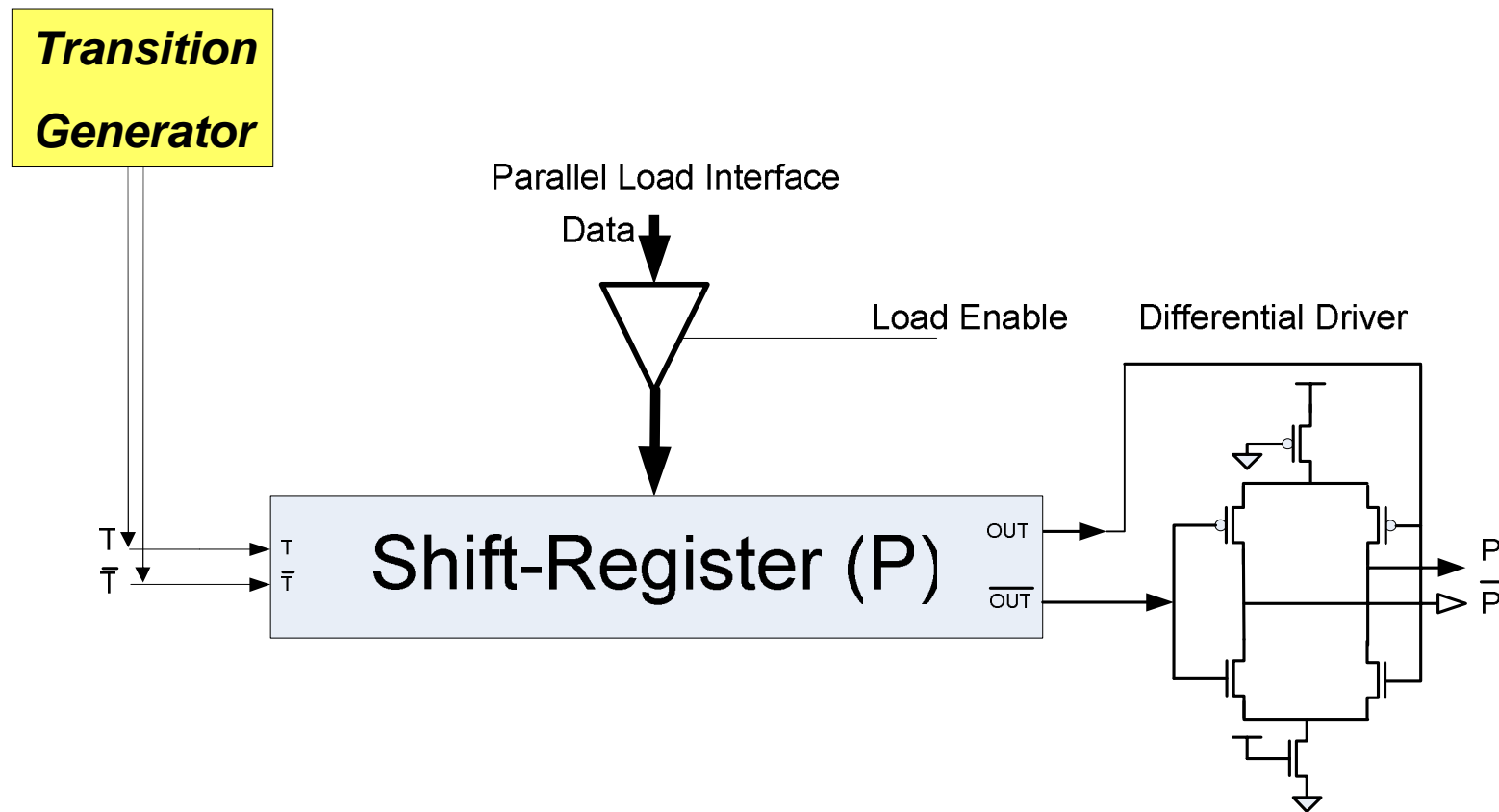

- Same circuit drives  $S$ ,  $\bar{S}$  lines




# RX – De-Serializer and Decoder

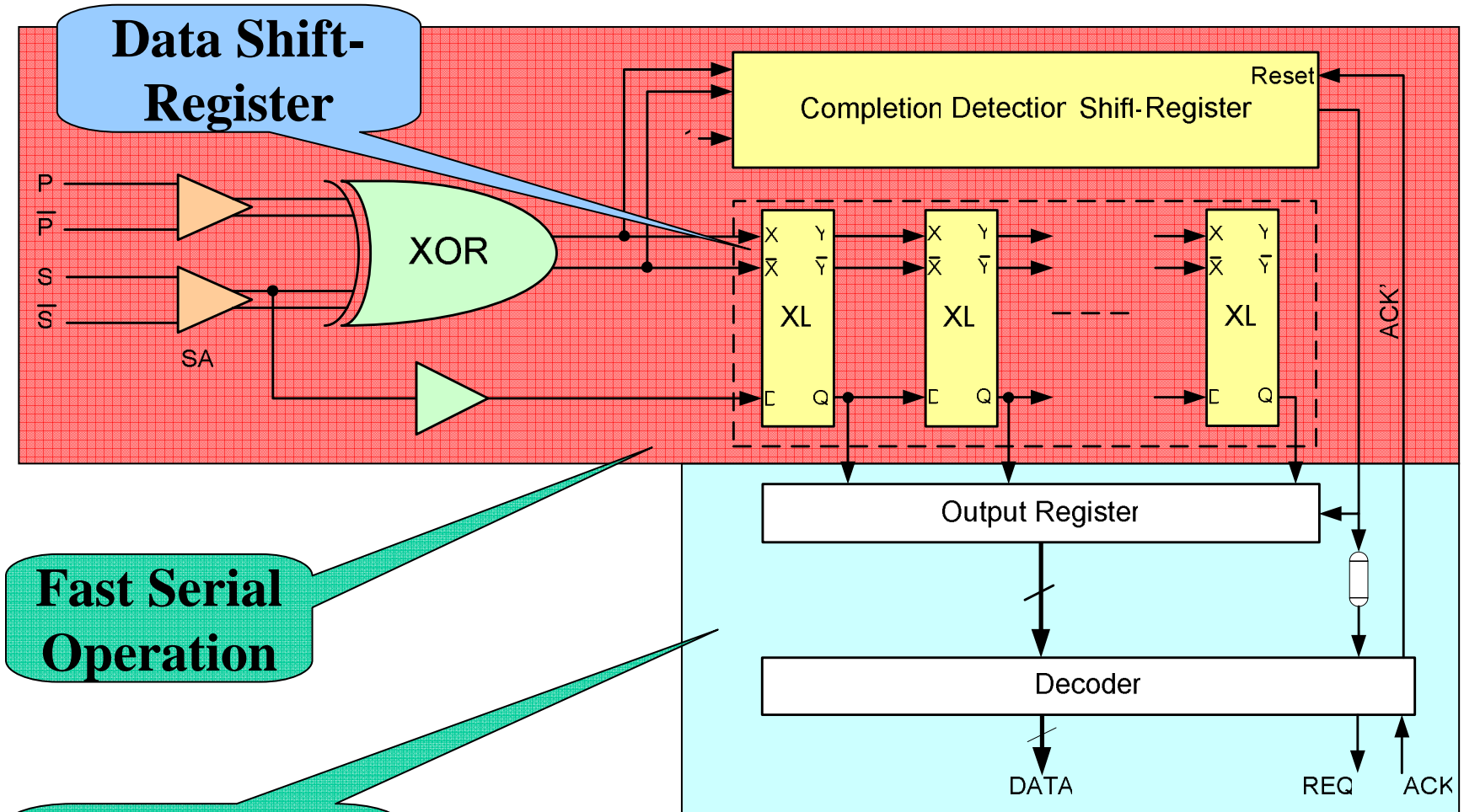




# Fast Asynchronous Shift Register

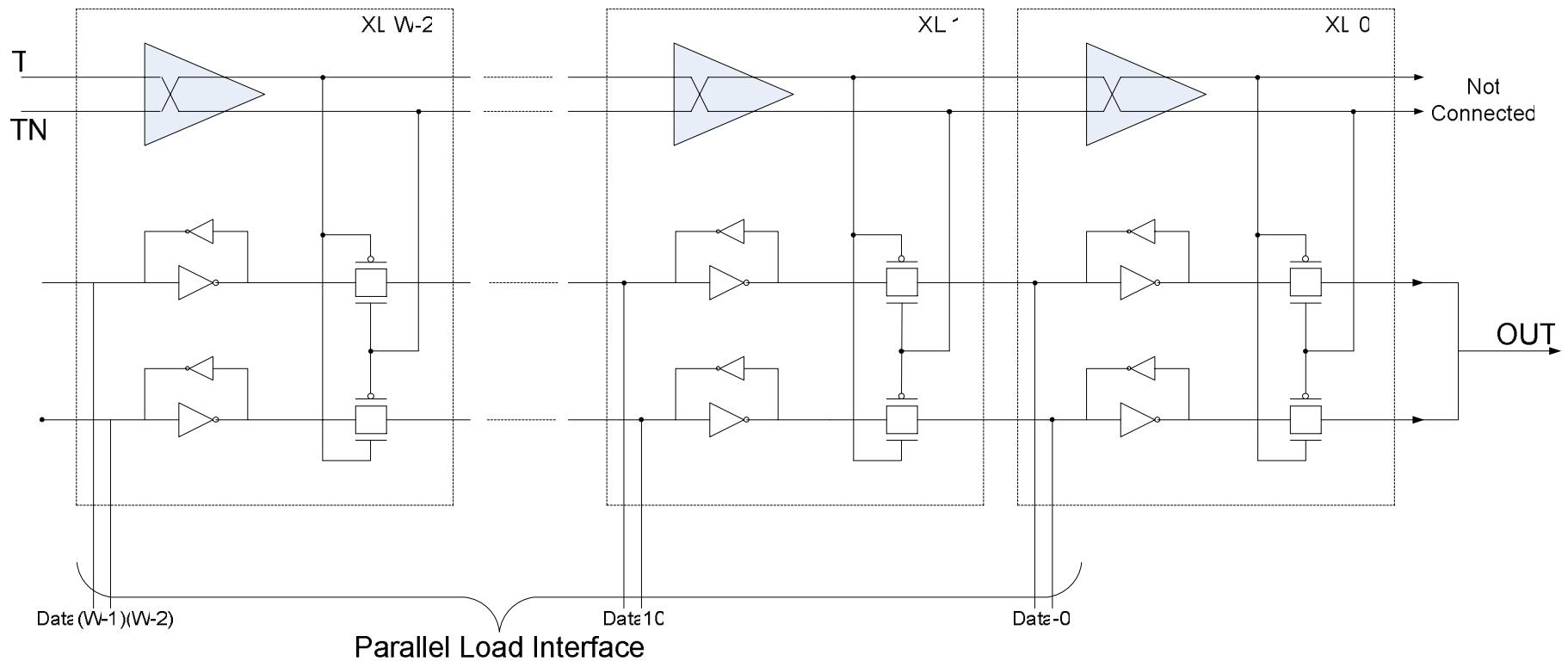





# Shift-Register Configurations

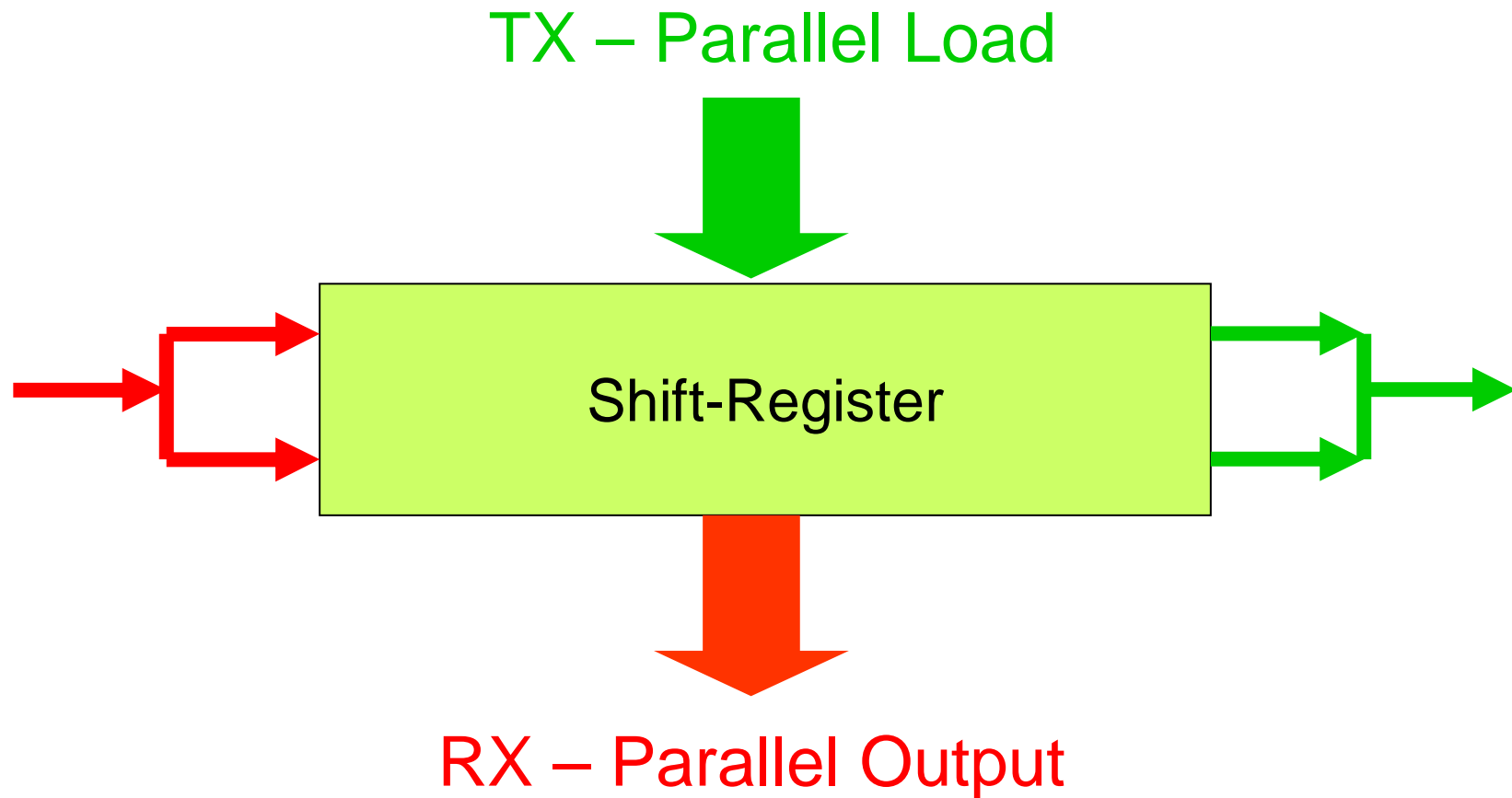



# Circuitry & Performance

  

- For typical conditions SR worked down to 14ps data cycle (71Gbps)
- Data is shifted inside sub-pipes twice slower than transition rate





# Performance

- SPICE simulation show correct operation at target data cycle of 15ps
- SR is asynchronous – allows non-uniform delay intervals between successive bits



- Verified at 24 PVT corners (0.7-1.35V, -10-110°C)
- Verified up to  $10\sigma$  in-die variation in  $L_{\text{EFF}}$  and  $V_T$  (Monte-Carlo simulations)



# Conclusions

- Novel Asynchronous Communication scheme
  - Wave-pipelining over the channel
  - Word-acknowledgement instead of bit-acknowledgement
  - LEDR encoding and differential signaling
- Fast serializers and de-serializers
  - Based on the fast shift register
- Data cycle of a single FO4 inverter delay
  - 15ps on 65nm process, 67 Gbps
- Robust to in-die variations
  - Thanks to asynchronous design
- The fast SERDES is useful for high-bandwidth long on-chip interconnects, where bit serial communication is preferred thanks to reduced area, easier routing and reduced leakage